



**POLITECNICO
DI MILANO**

www.polimi.it



STM32 – SPI


Ing. Arianna De Vecchi, Prof. Federica Villa



Serial Peripheral Interface

=

 Synchronous serial communication interface used for short-distance communication




Full-duplex (bidirectional) communication using a single-master multi-slave architecture.

Slaves are individually selected by means of the **Slave Select (SS)** – also called **Chip Select (CS)** – line, asserted by the master. Often, these lines are active LOW, as indicated by the overbar: the line must be pulled LOW to enable the selected slave device.



SPI - Functionality

 

MOSI: Master Out, Slave In

MISO: Master In, Slave Out

SCLK: Serial Clock

Transmissions normally involve two shift registers of some given word-size, such as eight bits. During each clock cycle, the master sends a bit on the MOSI line and the slave reads it. At the same time, the slave outputs a bit on the MISO line and the master reads it (“virtual ring topology”)

Data is shifted out MSB first.




How many wires?

Often called '4-wires protocol'



but you don't always need 4 wires!

 


...but often components have other auxiliary pins, that might be synchronous to the SCLK or not. E.g. :

- Reset (sync or async)
- Output enable (OE)
- ...



Multi-slave configurations


 


Independent slaves:

Every slave has an independent SS line.
Requires the slave to enter a tri-state (high-impedance) mode of its MISO output when not selected.



Multi-slave configurations

  

Daisy chain:

A single SS line is shared by all devices. Communication is handled like a shift register.

When transmitting data to a specific peripheral on the SPI bus, ensure that the total data length matches the number of peripherals in the chain. To prevent disrupting the operation of other peripherals, send No Operation (NOP) or idle commands to the devices not being targeted.



Clock POLarity & Clock PHase

Clock Polarity (CPOL):

This determines the **idle state of the clock signal (SCK)**:



- **CPOL = 0**: The clock is idle when it is **low**.
- **CPOL = 1**: The clock is idle when it is **high**.

When communication begins, the clock toggles between its idle state and the active state. This edge will be referred to as the leading (first) edge, while the other one will be referred to as the trailing (second) edge.

Clock Phase (CPHA):

This determines **when the data is sampled (read)** relative to the clock transitions:

  - **CPHA = 0**: Data is sampled on the leading edge.
- **CPHA = 1**: Data is sampled on the trailing edge.





SPI mode

The combination of CPOL and CPHA results in four SPI modes:

Mode	CPOL	CPHA	Clock Idle State	Sampling Edge	Shifting Edge
0	0	0	Low	Rising edge (first)	Falling edge (second)
1	0	1	Low	Falling edge (second)	Rising edge (first)
2	1	0	High	Falling edge (first)	Rising edge (second)
3	1	1	High	Rising edge (second)	Falling edge (first)

 


Figure 1. SPI Mode 0, 0



Pros:



- Full duplex communication
- Push-pull drivers provide good signal integrity (and high speed)
- **Higher speed** compared to I2C
- Complete protocol flexibility (not limited to 8-bit words)
- Very simple hardware interface
 - Often less circuitry, hence less power dissipated
 - Slaves don't need oscillators
- Very simple software implementation

Cons:

- Requires **more pins** on IC packages than I2C
- No hardware slave acknowledgment (the master could be transmitting to nowhere and not know it)
- Typically supports only one master device (depends on device's hardware implementation)
- Only handles short distances
- Many existing variations, making it difficult to find development tools like host adapters that support those variations

:

  4 wire synchronous full-duplex communication
(up to 42Mbit/s at $f_{CPU} = 84 \text{ MHz}$)



- SPI1 and SPI4 can communicate at up to 42 Mbit/s, SPI2 and SPI3 can communicate at up to 21 Mbit/s.
- The 3-bit prescaler gives 8 master mode frequencies and the frame is configurable to 8 bits or 16 bits.
- All SPIs can be served by the DMA controller.



SPI configuration

Configuration

Reset Configuration

✓ Parameter Settings

✓ User Constants

✓ NVIC Settings

✓ DMA Settings

✓ GPIO Settings

Configure the below parameters :

Basic Parameters

Frame Format

Motorola

Data Size

8 Bits

First Bit

MSB First

Clock Parameters

Prescaler (for Baud Rate)

~~2~~ 4

Clock Polarity (CPOL)

Low

Clock Phase (CPHA)

1 Edge

Advanced Parameters

CRC Calculation

Disabled

NSS Signal Type

Software



HAL_StatusTypeDef HAL_SPI_Transmit (SPI_HandleTypeDef *hspi, uint8_t * pData, uint16_t Size, uint32_t Timeout)

Transmit an amount of data in blocking mode.

Parameters:

hspi: pointer to a SPI_HandleTypeDef structure that contains the configuration information for SPI module.

pData: pointer to data buffer

Size: amount of data to be sent

Timeout: timeout duration

HAL_StatusTypeDef HAL_SPI_Transmit_DMA (SPI_HandleTypeDef *hspi, uint8_t * pData, uint16_t Size)

Transmit an amount of data in non-blocking DMA mode.

8-bit serial-in, parallel-out shift registers

Connections:

- **Serial Data Input (DS):** This pin receives the serial data from the microcontroller.
- **Shift Clock (SH_CP):** This clock input shifts the data into the shift register. On each rising edge of this clock, the data on the **DS** pin is shifted into the shift register.
- **Store Clock (ST_CP):** This clock is used to latch the shifted data into the output registers (the parallel outputs). The data in the shift register is transferred to the output pins on the rising edge of this clock.
- **OE (Output Enable):** This pin controls whether the parallel outputs (**Q0-Q7**) are enabled. When **OE** is **LOW**, the outputs are enabled and show the values stored in the shift register. When **OE** is **HIGH**, the outputs are disabled (set to high impedance, Hi-Z).
- **Output Pins (Q0 - Q7):** These are the 8 parallel output pins that represent the data in the shift register once it has been latched.
- **Q7S (Serial Out):** This pin provides the serial bit output from the shift register, corresponding to the last bit (**Q7**) in the shift register. This pin can be used to chain multiple shift registers, sending the serial bit from **Q7S** of one 74HC595 to the **DS** input of another 74HC595.
- **Reset Pin (MR):** This pin resets the shift register to zero when activated.



 
 


Fig. 4. Logic diagram

 

LED Matrix – Shift Register

 
- The SNx4HC595 is part of the HC family of logic devices intended for CMOS applications.



- Is an 8-bit **shift register** that feeds an 8-bit D-type **storage register**.
- Both the shift register clock (**SRCLK**) and storage register clock (**RCLK**) are positive-edge triggered.
- The storage register has parallel 3-state outputs. Separate clocks are provided for both the shift and storage register.
- The shift register has a direct overriding clear (**SRCLR**) input, serial (**SER**) input, and serial outputs for cascading. When the output-enable (**OE**) input is high, the outputs are in the high-impedance state.



Table 1. Function Table

INPUTS					FUNCTION
SER	SRCLK	SRCLR	RCLK	OE	
X	X	X	X	H	Outputs $Q_A - Q_H$ are disabled.
X	X	X	X	L	Outputs $Q_A - Q_H$ are enabled.
X	X	L	X	X	Shift register is cleared.
L	↑	H	X	X	First stage of the shift register goes low. Other stages store the data of previous stage, respectively.
H	↑	H	X	X	First stage of the shift register goes high. Other stages store the data of previous stage, respectively.
X	X	X	↑	X	Shift-register data is stored in the storage register.

 


Column Driver


LED Matrix Configurations

  

Row Driver

 

Column Driver

 

- Transistors as voltage controlled switches
- Transistor is turned on, the common cathodes of the selected column are connected to ground and the chosen LEDs light up


Data transfer to the led matrix(1)

16 clock pulses to transfer the data to the led matrix (daisy chain configuration – Most significant bit)


8 clock pulses:

- Transfer the row data in the row shift register
- Write the column data in the column shift register


OE – OUTPUT ENABLE

 

ROW
SHIFT REGISTER

 


COLUMN
SHIFT REGISTER

 

For each column the correct row data are written



Data transfer to the led matrix(2)

 

1
0
0
0
1
0
0

{ 68 , 16 }

MULTIPLEXING:

You can only write
ONE COLUMN AT A TIME!

To show a complete matrix,
quickly **scan through all
columns, writing one
column at a time**, with a
fast refresh rate (> 50 Hz)

i.e. one column every < 4 ms

row	column
.	16
.	8
.	4
.	2
.	1



5 × 7 font example

5 × 7


A B C D E F G H I J K L M

N O P Q R S T U V W X Y Z

1 2 3 4 5 6 7 8 9 0



LED matrix computation

 

How to use the
LED matrix computation.xlsx
file

5 × 7 LED matrix design

	16	8	4	2	1	
			X			64
		X		X		32
	X				X	16
	X				X	8
	X	X	X	X	X	4
	X				X	2
	X				X	1

Computed value

COL	16	8	4	2	1
ROW	31	36	68	36	31

Instruction:

Write an 'x' (small letter) where you want the LED to light up.

The corresponding pairs of row and column data appears in the cells in RED (format: decimal)



Objective

Transmit a letter to the LED matrix using SPI and a timer interrupt & Alternate between two letters (or one letter and one symbol)

Use the SPI DMA write and avoid the Hal_Delay function.



Project hints

- Identify the SPI data and clock pins, as well as the RCLK of the register
- Setup a timer to provide an interrupt every 4 ms. In the callback, write one column of the LED matrix and pulse the RCLK. After writing the 5th column, roll over to the first one.
- Enable the SPI_TX DMA transfer. Beware of how the SPI DMA transfer works.
- Find a way to change what is shown on the matrix. Keep the interrupt routine code as simple as possible.
- Compile and debug the code.